


Name: ZHOU Siyu Student ID: Marks: / 100

- This is an **individual** quiz.
- Please submit the **soft copy** of your answer to Blackboard (as a doc/docx/pdf file).

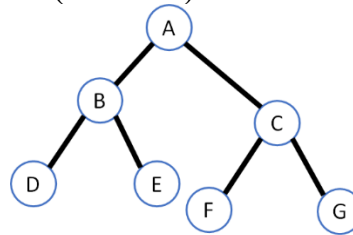Question 1

[40 marks]


- 1(a)** Traverse the following Binary Search Tree (BST). List the *in-order* (5 marks), *pre-order* (5 marks) and *post-order* (5 marks) of the traversal.



In-order: D, B, E, A, F, C, G
Pre-order: A, B, D, E, C, F, G
Post-order: D, E, B, F, G, C, A

- 1(b)** Use the postfix expression below to form a binary tree (15 marks), then write the prefix form (5 marks) and the infix form (5 marks) of this tree.

ED-CBA+* *

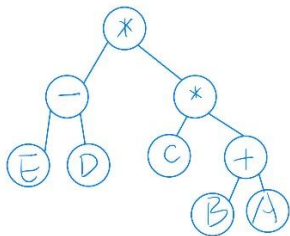


Prefix: *-ED*C+BA
Infix: (E-D) *(C*(B+A))

Question 2

[60 marks]


This question is about Boolean algebra and circuits.

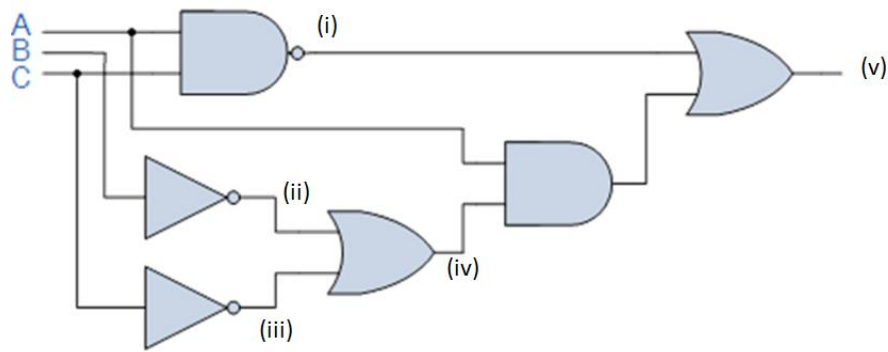- 2(a)** Write down the logic expression at the points (i) to (v) for the following circuit. (15 marks).



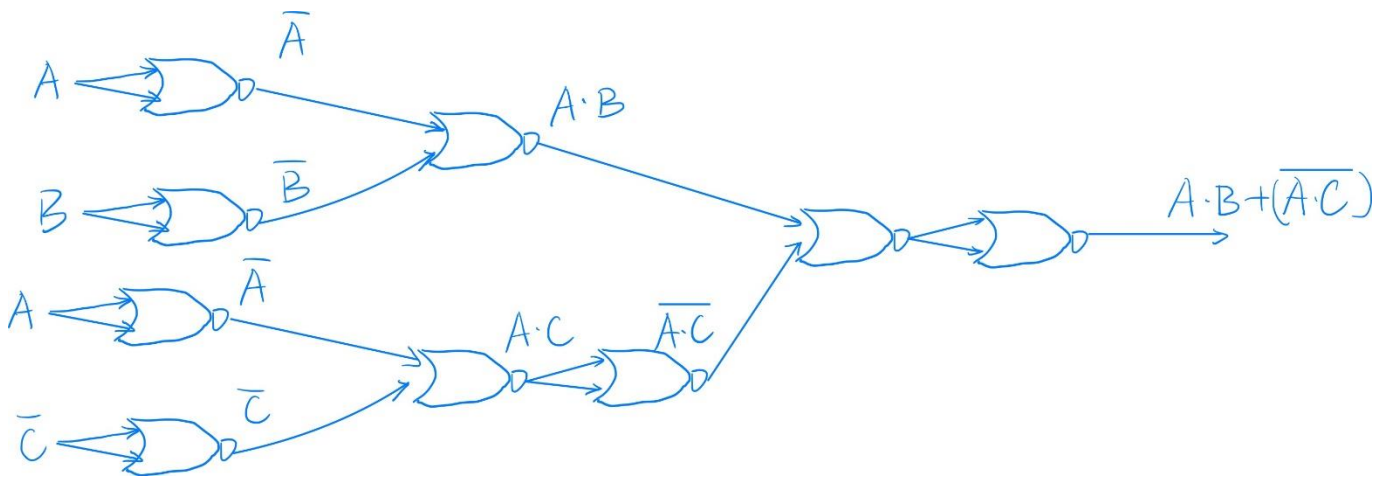- (i) $A \text{ NAND } C$
- (ii) $\text{NOT } B$
- (iii) $\text{NOT } C$
- (iv) $(\text{NOT } B) \text{ OR } (\text{NOT } C)$
- (v) $(A \text{ NAND } C) \text{ OR } (A \text{ AND } (\text{NOT } B) \text{ OR } (\text{NOT } C))$

2(b) Express $F(A, B, C) = A \cdot B + (\overline{A} \cdot \overline{C})$ by using a combinational circuit with NOR gates only (20 marks)



2(c) Simplify the following expression using K-map (25 marks)

$$F(A, B, C) = A\overline{B}C + \overline{A}BC + AB + \overline{A}\overline{B}C$$

$$AB = ABC + AB\overline{C}$$

K-map:

	BC	$B\overline{C}$	$\overline{B}\overline{C}$	$\overline{B}C$
A	1	1		1
\overline{A}	1			1

Then

$$F(A, B, C) = C + AB\overline{C}$$